


# Differential Amplifier

PAGE No.

DATE

/ /

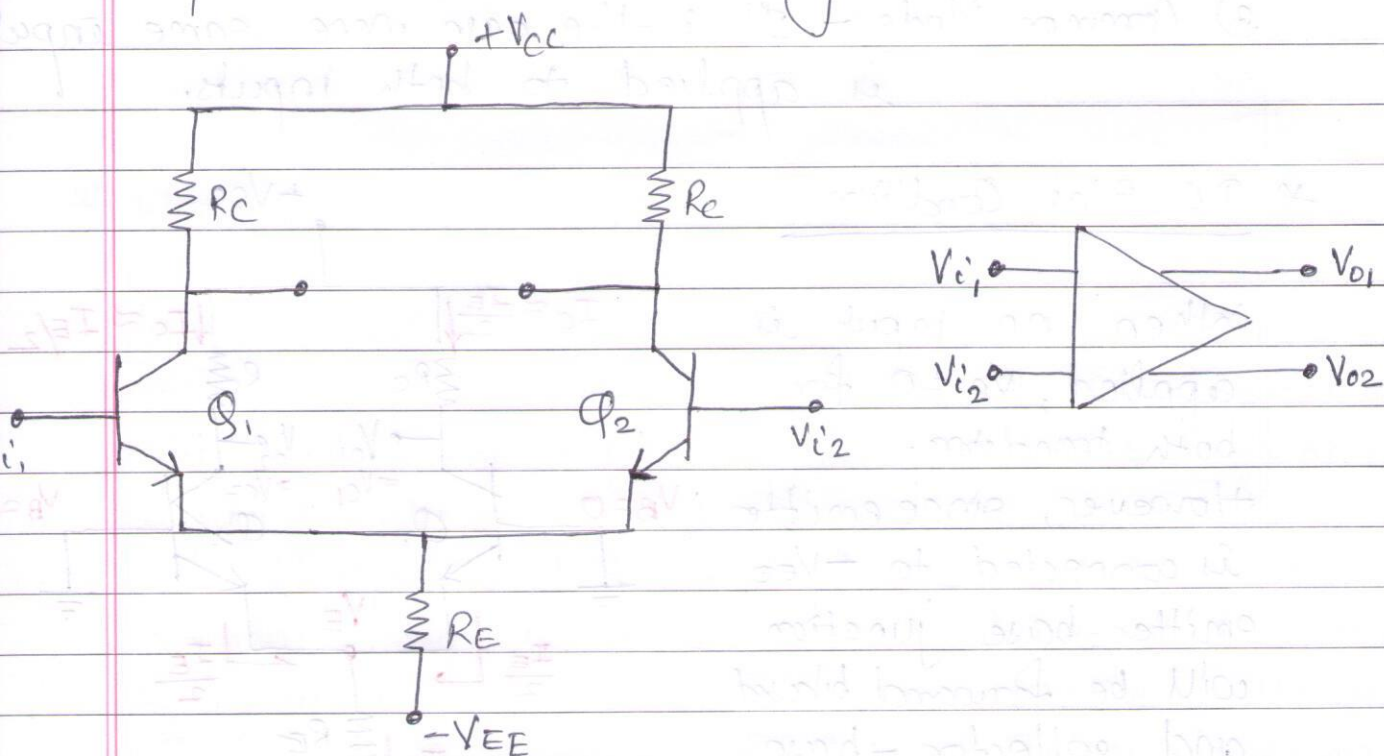The differential amplifier circuit is an extremely popular connection used in IC units. A basic differential amplifier circuit and its symbol is shown below.



It consists of two transistors  $Q_1$  and  $Q_2$  well matched (i.e.  $\beta_1 = \beta_2 = \beta$ ) connected in common emitter configuration with emitters connected together. Notice that the circuit has two separate inputs and two separate outputs. Typically it has two separate supply voltages, however, the circuit can also operate with single supply.

## \* Types of input signal combinations:-

A number of input signal combinations are possible for a differential amplifier.


1) Single ended - An input signal is applied to either input with the other input connected to ground.

- 2) Double ended - If two opposite polarity signals are applied, the operation is referred as double ended.
- 3) Common Mode - It is the case where same input is applied to both inputs.
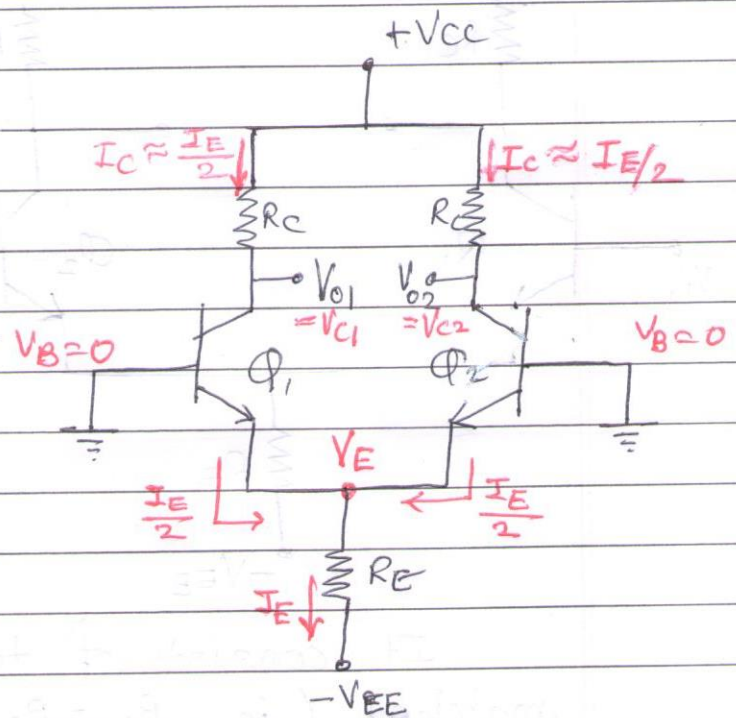
### \* DC Bias Condition

When no input is applied,  $V_B = 0$  for both transistors.

However, since emitter is connected to  $-V_{EE}$ , emitter-base junction will be forward biased and collector-base junction is reverse biased.



$$\Rightarrow V_E = 0V - V_{BE} = -0.7V$$

$\therefore$  Emitter d' bias current is

$$I_E = \frac{V_E - (-V_{EE})}{R_E} = \frac{-0.7 + V_{EE}}{R_E} \quad \text{--- (1)}$$

$$= \frac{V_{EE} - 0.7}{R_E} \quad \text{--- (2)}$$

Since, the transistors are well matched, we have

$$\beta_1 = \beta_2 = \beta$$

$$\Rightarrow I_{C1} = I_{C2} = \frac{I_E}{2} \quad \text{--- (3)}$$



∴ Collector voltage is

$$V_{c1} = V_{c2} = V_{CC} - I_C R_C$$

$$= V_{CC} - \frac{I_E R_C}{2} \quad \rightarrow \text{M} \rightarrow \text{④}$$


## \* Working

### ① Single ended input -


When a diff-amp is operated in this mode, one input is grounded and the signal is applied only to the other input.

If the signal is applied to input 1, an inverted, amplified signal voltage appears at output 1. Also, a signal voltage appears in phase at the emitter of  $Q_1$ . Since the emitters of  $Q_1$  and  $Q_2$  are common, the emitter signal becomes an input to  $Q_2$ , which functions as a common-base amplifier. The signal is amplified by  $Q_2$  and appears non-inverted at output 2. This action is illustrated in part (a).

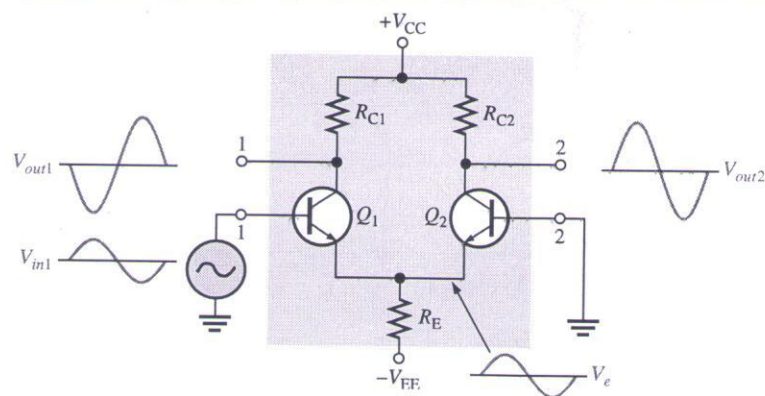In the case where the input is applied to input 2, with input 1 grounded, an inverted, amplified




(a)

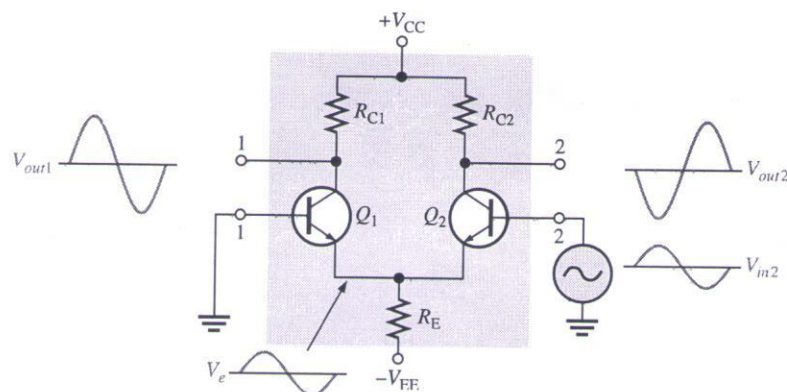


(b)

signal voltage appears at output 2. In this situation  $Q_1$  acts as a common-base amplifier and a non-inverted amplified signal appears at output 1. This action is illustrated in part (b) of the figure.


## ② Differential mode —

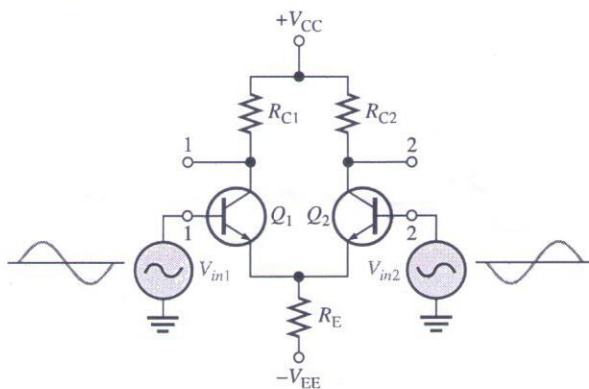

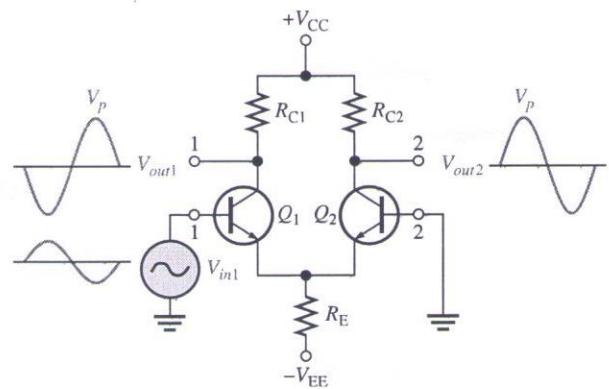
(a) Differential inputs ( $180^\circ$  out of phase)



(b) Outputs due to  $V_{in1}$

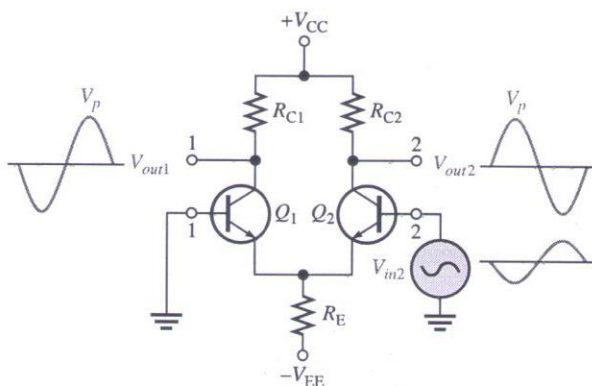

(c) Outputs due to  $V_{in2}$

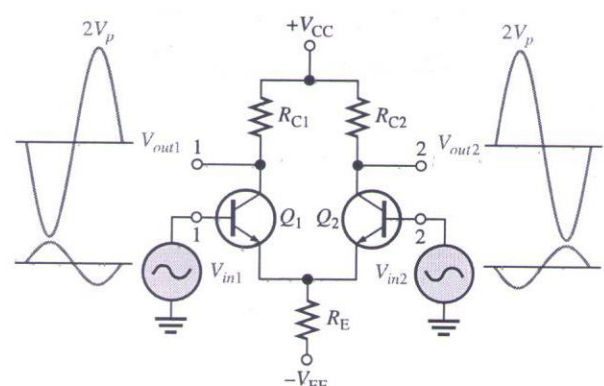

(d) Total outputs

In this mode, two opposite-polarity (out of phase) signals are applied to the inputs, as shown in figure (a). This type of operation is also referred as **double-ended**. Each input affects the outputs as follows:

- i) Figure (b) shows the output signals due to the signal on input 1 acting alone as a single-ended input
- ii) Figure (c) shows the output signals due to the




single signal on Input 2 acting alone as a single-ended input.


iii) Notice that in parts (b) and (c), the signals on output 1 are of the same polarity. The same is true for output 2.

iv) By superpositioning both output 1 signals and both output 2 signals, we get the differential operation, as pictured in Figure (d).


### ③ Common - Mode :-

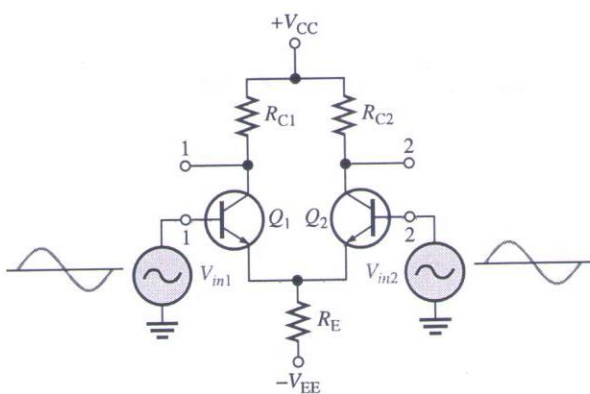


(a) Common-mode inputs (in phase)

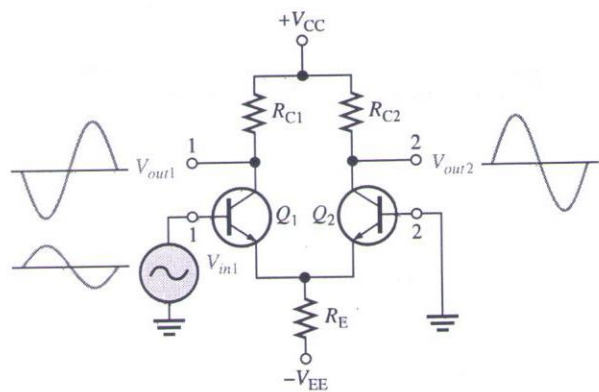

(b) Outputs due to  $V_{in1}$

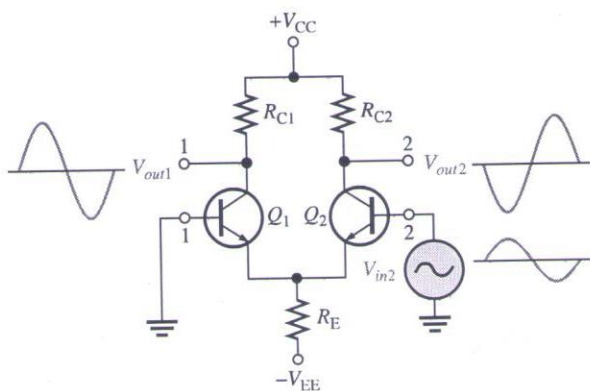

(c) Outputs due to  $V_{in2}$

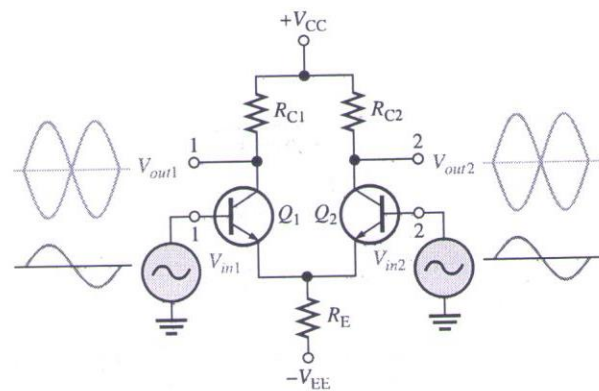

(d) Outputs due to  $V_{in1}$  and  $V_{in2}$  cancel because they are equal in amplitude but opposite in phase. The resulting outputs are 0 V ac.

One of the most important aspect of the operation of a diff-amplifier can be seen by considering the **common-mode**. In this case the ~~same~~ signal with same phase, frequency and amplitude is applied



to the two inputs. Figure (b) shows the output signals due to the signal on only input 1. Figure (c) shows the output signals due to the signal on only input 2. Notice that the corresponding signals on output 1 are of the opposite phase of that on output 2. When both the inputs are applied, the outputs are superimposed and they cancel, resulting in the zero output voltage, as shown in figure (d). This action is called **Common-Mode Rejection**.

### # COMMON-MODE REJECTION RATIO (CMRR):-

In most of practical operations, differential amplifier is used in single-ended or in differential mode. The desired signal appears only on one input or with opposite polarities on both input lines. These desired signals are amplified and appear on the outputs. ~~When~~ An unwanted signal (noise) appearing with the same polarity on the both inputs, are essentially ~~and~~ cancelled by differential amplifier and do not appear at the outputs. This is called common mode rejection.

**CMRR (Common Mode Rejection Ratio)** is the measure of an amplifier's ability to reject common-mode signals. Ideally, a differential amplifier provides a very high gain for desired signals (single-ended or differential) and zero gain for common-mode signals. Practically they do exhibit a very small common-mode



gain (usually much less than 1), while providing a high differential voltage gain (usually several thousands). If  $A_{vd}$  is the differential voltage gain and if  $A_{cm}$  is the common-mode gain, the CMRR is defined as

$$CMRR = \frac{A_{vd}}{A_{cm}}$$

The higher the CMRR, the better. A very high value of CMRR means that the differential gain  $A_{vd}$  is high and common-mode gain  $A_{cm}$  is low.

### Techniques to improve CMRR :-

#### ① Use of Constant-Current Source :-

To achieve high CMRR, use of constant-current source is a popular choice. Figure (a) shows a differential amplifier with a constant-current source circuit to provide a large

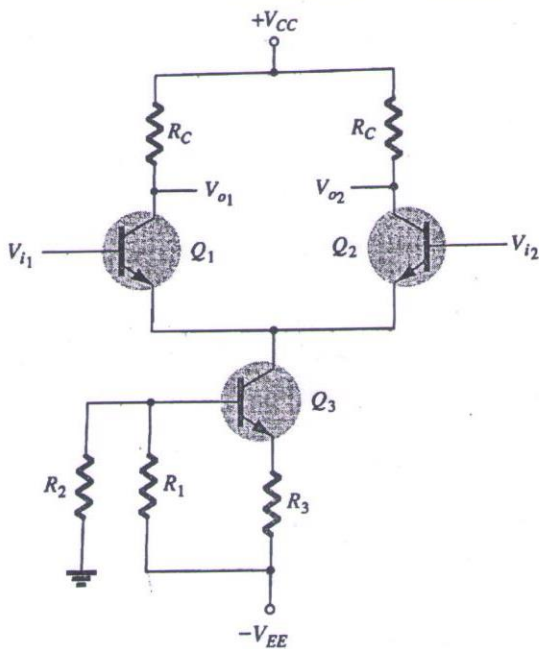


FIG. (a)

Differential amplifier with constant-current source.


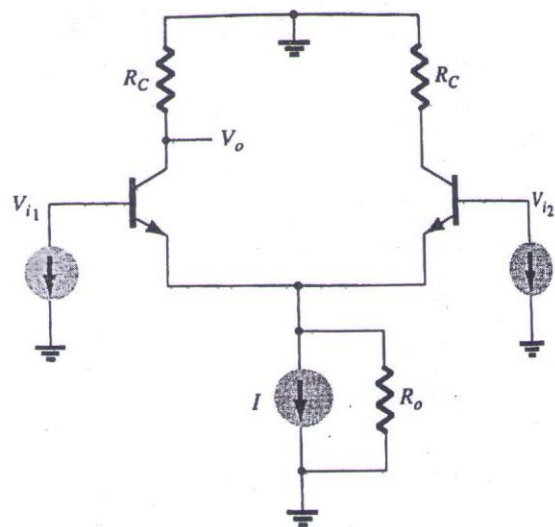


FIG. (b)

AC equivalent of the circuit of Fig. (a)

value of resistance from common emitter to ac ground. The corresponding ac equivalent is shown in Figure (b). A partial constant-current source is shown as a high impedance, in parallel with constant current.

## ② Use of Current Mirror -

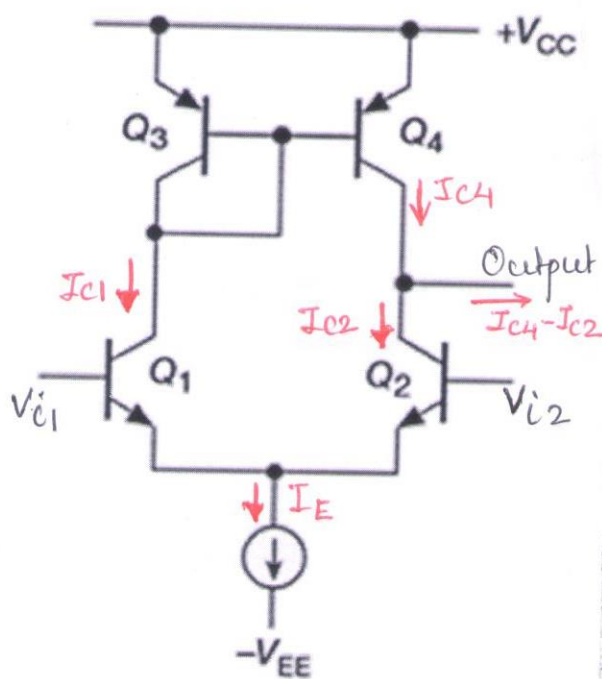

Though the  $Q_1$  and  $Q_2$  are very closely balanced, small variations in their parameters leads to increase in common-mode gain. Therefore, to improve circuit performance a self-balancing circuit using current mirror is employed.

Here  $Q_3$  and  $Q_4$  form a current mirror of their own. As a result, the reference current for  $Q_3$  is exactly same to the collector current of  $Q_1$ . This current

is mirrored by  $Q_4$  and has no other connection.

When  $V_{i1} = V_{i2}$ , there is no differential input. This means that  $I_{C1} = I_{C2}$ .  $Q_3$  uses  $I_{C1}$  as its reference current, and this current is mirrored by  $Q_4$ . Therefore  $I_{C4} = I_{C2}$  and there is no current flowing into or out of output.

Now, consider  $V_{i1}$  increase, which increases  $I_{C1}$  by  $0.1\text{mA}$ . This increases  $I_{C3}$  by  $0.1\text{mA}$ , which in turn increases  $I_{C4}$  by  $0.1\text{mA}$ . At the same time, increasing  $I_{C1}$  by  $0.1\text{mA}$  also means that decreasing



$I_{C2}$  by  $0.1\text{mA}$ . As a result, there is now a difference of  $0.2\text{mA}$  between  $I_{C2}$  and  $I_{C4}$ . This becomes the output current.

If we apply a differential input sufficient to increase  $I_{C2}$  by  $0.1\text{mA}$ , the same thing happens in reverse.  $I_{C1}$  decreases by  $0.1\text{mA}$ , thus decreasing  $I_{C3}$  by  $0.1\text{mA}$  and  $I_{C4}$  by  $0.1\text{mA}$ . This creates a  $0.2\text{mA}$  difference in the other direction between  $I_{C2}$  and  $I_{C4}$ . Again that difference becomes the output current.

This increases differential gain and thus improves CMRR.